

BBM233: Logic Design Lab  
2023 Fall  
Board Experiment #(1) Report

Yusuf Küçüköner, 2210356092

October 25, 2023

## 1 Truth Table

<b>N</b>	<b>S</b>	<b>M</b>	<b>ALARM</b>
0	1	0	1
0	1	1	1
0	0	1	0
0	0	0	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Figure 1: Truth Table

From this truth table we get the equation by sum of products(Minterm method):  
 $\text{Alarm}(N,S,M) = N'SM + N'M'S + NMS$

## 2 Circuit and Efficiency

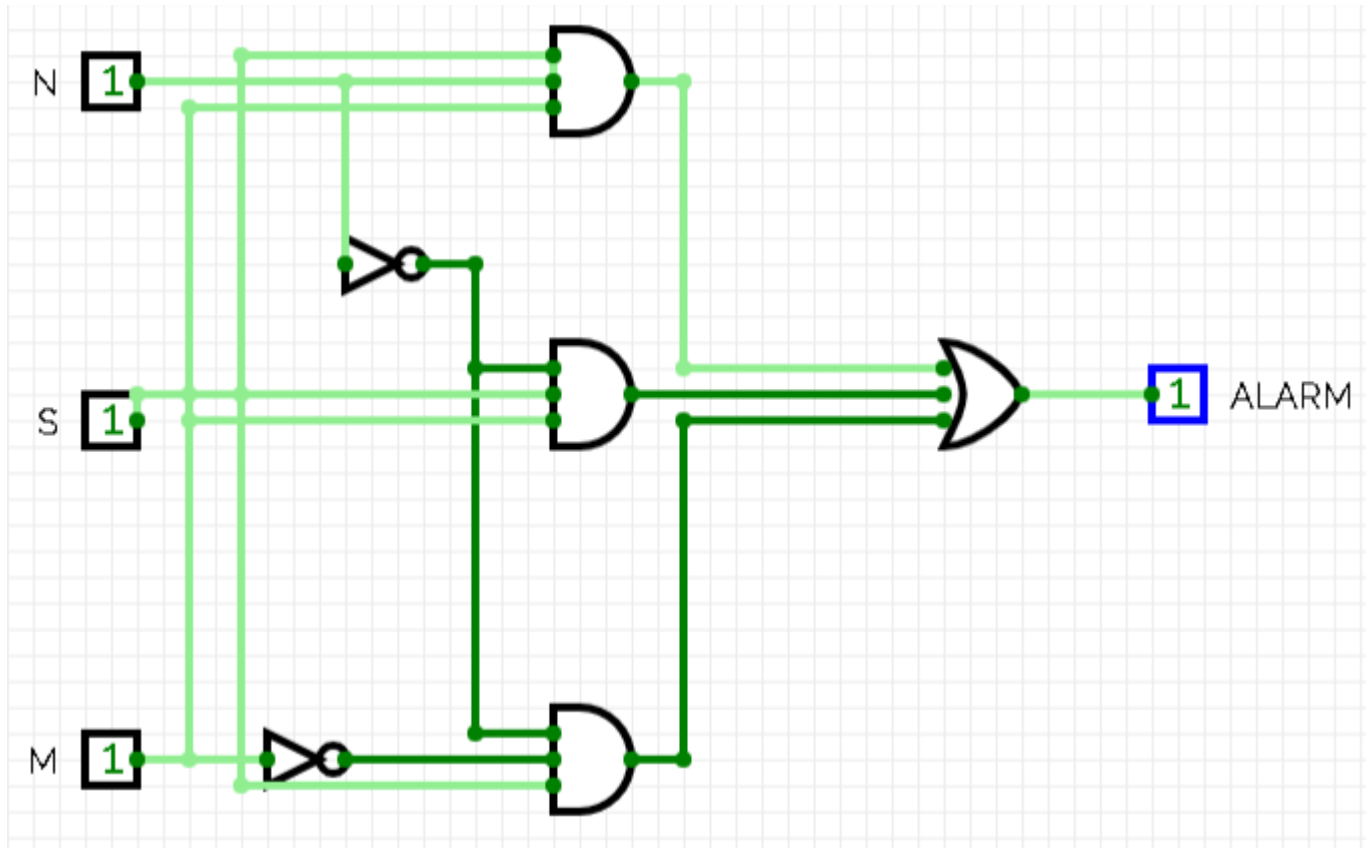


Figure 2: Circuit 1

This is the circuit of equation:  $\text{Alarm}(N,S,M) = N'SM + N'M'S + NMS$ , but the thing is we can simplify this equation and can make our circuit more efficient.

1.  $\text{Alarm}(N,S,M) = SM(N'+N) + SN'M'$
2.  $\text{Alarm}(N,S,M) = SM + SN'M' = S(M+N'M')$
3.  $\text{Alarm}(N,S,M) = S(M+(N+M)')$

This is more efficient formula which we only use 3 gates.

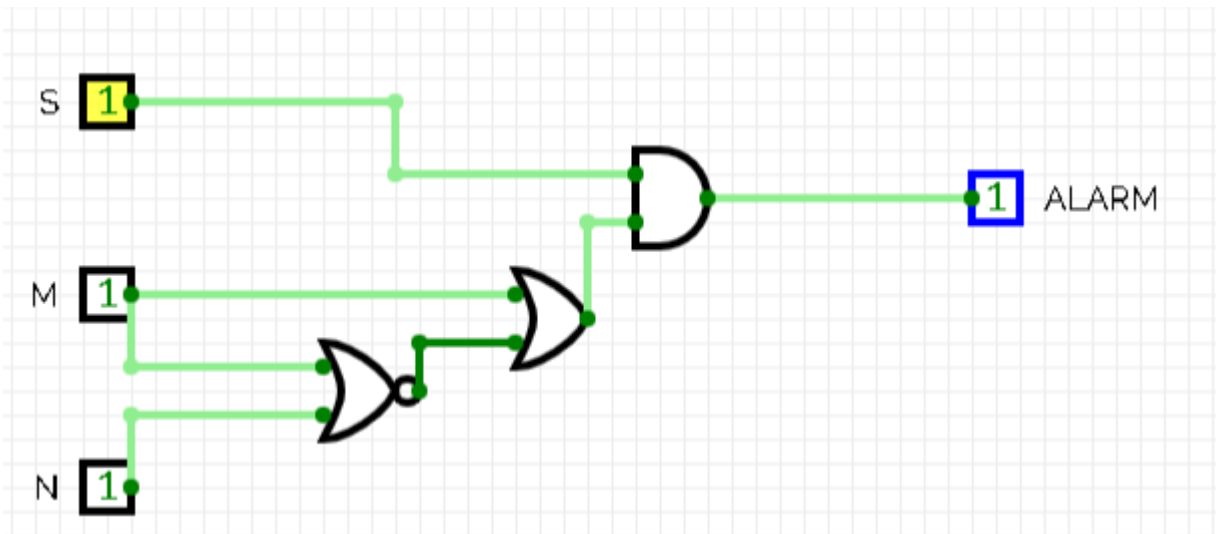


Figure 3: Circuit2